


Student Names: Emilcan Arıcan, M. Mustafa Küçük

Student IDs: 2016400231,2016400111


Session ID:21

Group ID:2

b)

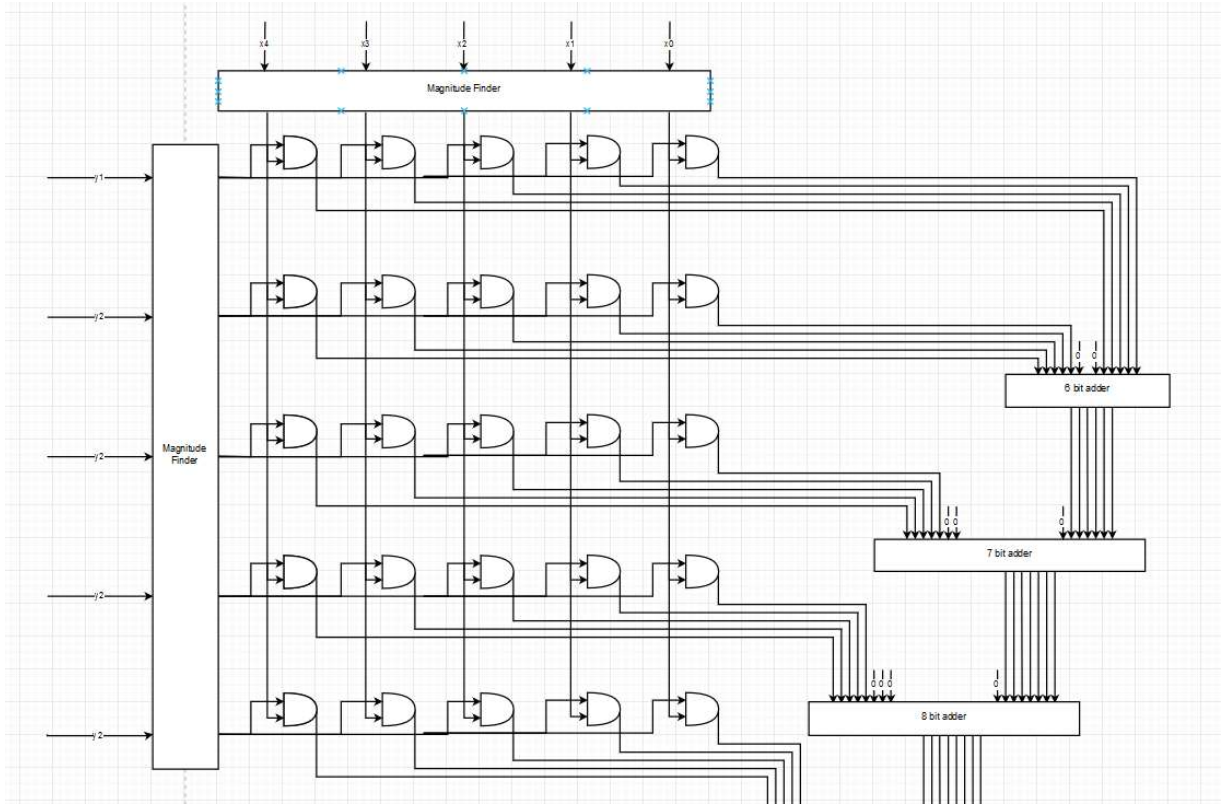

Group ID:2

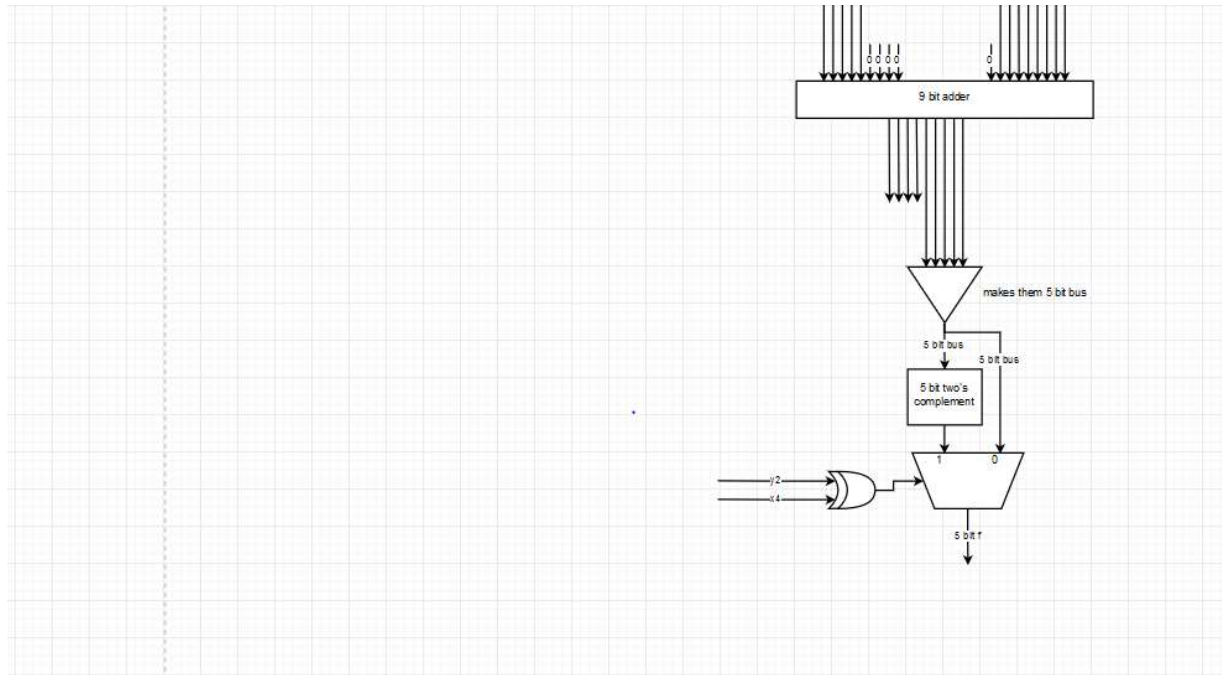

magnitude finder

5 bit a

5 bit complement

5 bit a'

Mux

5 bit magnitude of a

a4


Student Names: Emilcan Arıcan, M. Mustafa Küçük

Student IDs: 2016400231,2016400111


Session ID:21

Group ID:2

c)

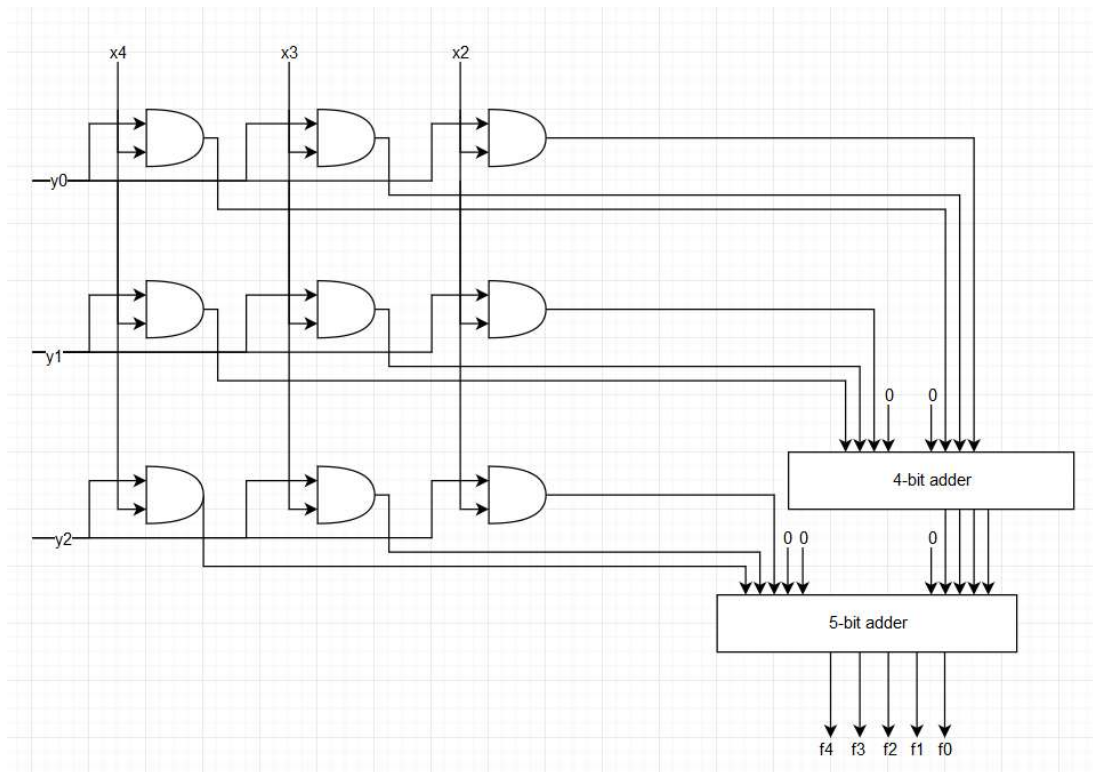

Inside Designs:

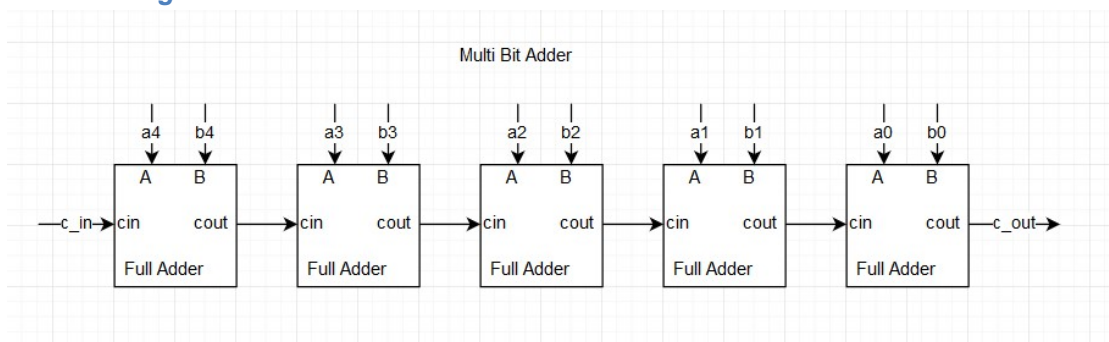


Student Names: Emilcan Arıcan, M. Mustafa Küçük

Student IDs: 2016400231,2016400111

Session ID:21

Group ID:2

d)

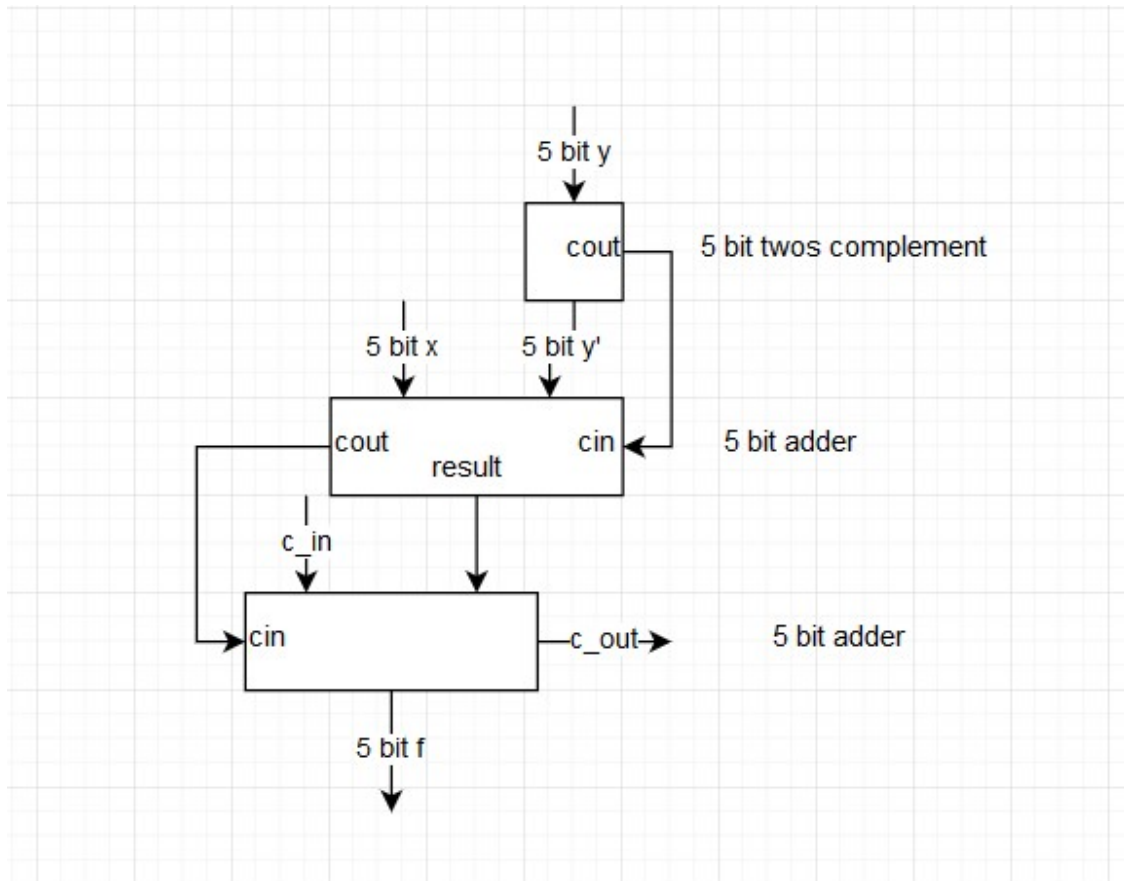


Inside Designs: (5 bit adders mentioned before)

Student Names: Emilcan Arıcan, M. Mustafa Küçük

Student IDs: 2016400231,2016400111

Session ID:21

Group ID:2

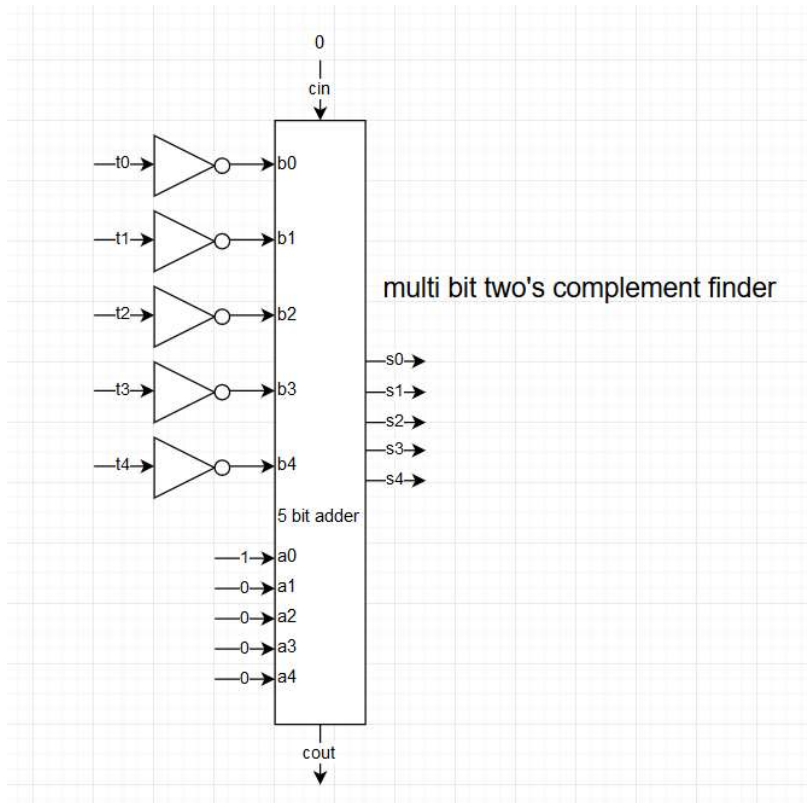

Step 2: Merge all operations with select inputs and organize outputs, Try to minimize your implementation by using repetitions, draw final circuit as the minimized final design of the ALU.

Student Names: Emilcan Arıcan, M. Mustafa Küçük

Student IDs: 2016400231,2016400111

Session ID:21

Group ID:2

